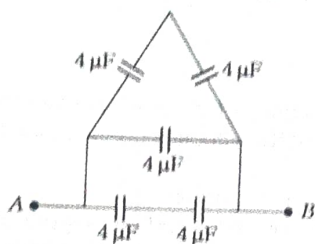


14. Equivalent capacitance between A and B is



- (a) $8 \mu\text{F}$ (b) $6 \mu\text{F}$
 (c) $26 \mu\text{F}$ (d) $\frac{10}{3} \mu\text{F}$
15. The energy stored in a capacitor of capacitance $100 \mu\text{F}$ is 50 J . Its potential difference is
 (a) 50 V (b) 500 V
 (c) 1000 V (d) 1500 V
16. The potential energy of a charged parallel plate capacitor is U_0 . If a slab of dielectric constant K is inserted between the plates, then the new potential energy will be
 (a) $\frac{U_0}{K}$ (b) $U_0 K^2$
 (c) $\frac{U_0}{K^2}$ (d) U_0^2
17. A series combination of n_1 capacitors, each of value C_1 , is charged by a source of potential difference 4 V . When

another parallel combination of n_2 capacitors, each of value C_2 , is charged by a source of potential difference V , it has the same (total) energy stored in it, as the first combination has. The value of C_2 , in terms of C_1 , is, then

- (a) $\frac{16C_1}{n_1 n_2}$ (b) $\frac{2C_1}{n_1 n_2}$
 (c) $16 \frac{n_2}{n_1} C_1$ (d) $2 \frac{n_2}{n_1} C_1$
18. If the charge on a capacitor is increased by 2 C , then the energy stored in it increases by 21% . The original charge on the capacitor is
 (a) 10 C (b) 20 C
 (c) 30 C (d) 40 C
19. A capacitor of capacitance value $1 \mu\text{F}$ is charged to 30 V and the battery is then disconnected. If it is connected across a $2 \mu\text{F}$ capacitor, then the energy lost by the system is
 (a) $300 \mu\text{J}$ (b) $450 \mu\text{J}$ (c) $225 \mu\text{J}$ (d) $150 \mu\text{J}$
 (e) $100 \mu\text{J}$
20. A parallel plate capacitor is charged to a potential difference of 50 volts . It is then discharged through a resistance for 2 seconds and its potential drops by 10 volts . Calculate the fraction of energy stored in the capacitance
 (a) 0.14 (b) 0.25
 (c) 0.50 (d) 0.64